



**Newcastle**  
University

# **An Adiabatic Power-Supply Controller for Asynchronous Logic Circuits**

P. Asimakopoulos and A. Yakovlev


The 20th UK Asynchronous Forum -  
The University of Manchester, 1st-2nd September 2008

# Summary


- Adiabatic logic background.
- Asynchronous adiabatic implementation.
- Simulations / Evaluation.
- Conclusions.

# Standard CMOS Energetics

1. Charging

 

2. Discharging

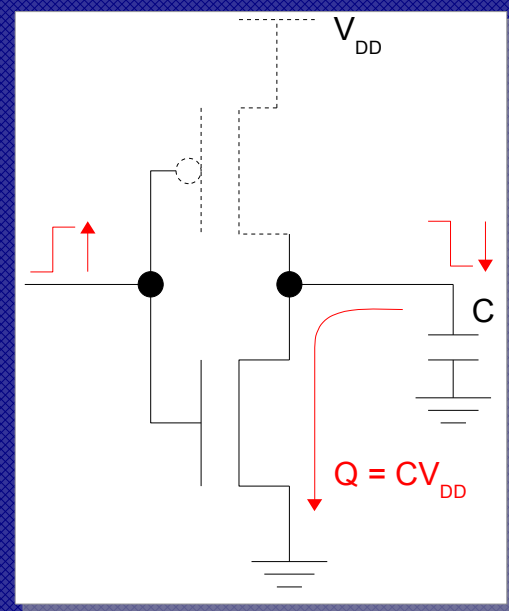

+

=>


$$E_d = QV_{DD} = CV_{DD}^2$$

The only ways to reduce energy consumption are:


1. Reduce supply voltage  $V_{DD}$ .
2. Reduce load capacitance  $C$ .

# Adiabatic Logic

## 1. Charging

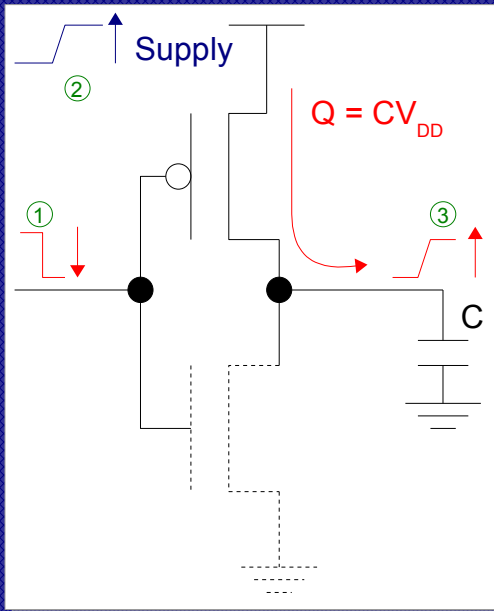


## 2. Discharging

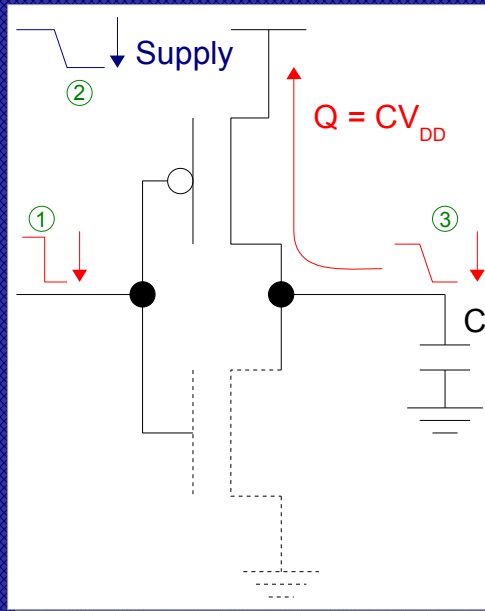

$\Rightarrow E_d = \text{very small}$

1. Charge  $Q$  is recovered back to the power supply.
2. Charging current becomes uniform and small over ramp time  $T \rightarrow$  energy dissipation is minimized.

# Adiabatic Logic

 


Voltage/Current/Energy measurements.


Dotted line: Conventional Inverter.  
Solid line: Adiabatic Inverter.

J S Denker, "A Review of Adiabatic Computing", 1994, IEEE Symposium on Low Power Electronics, pp.94-97.

# Adiabatic Logic

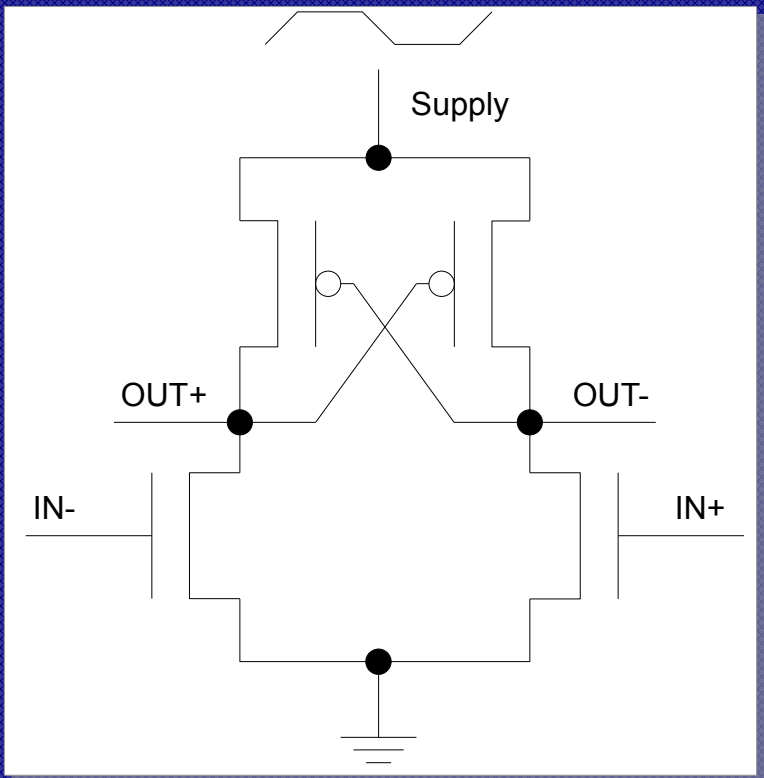


Basic 2N-2P Adiabatic Circuit.

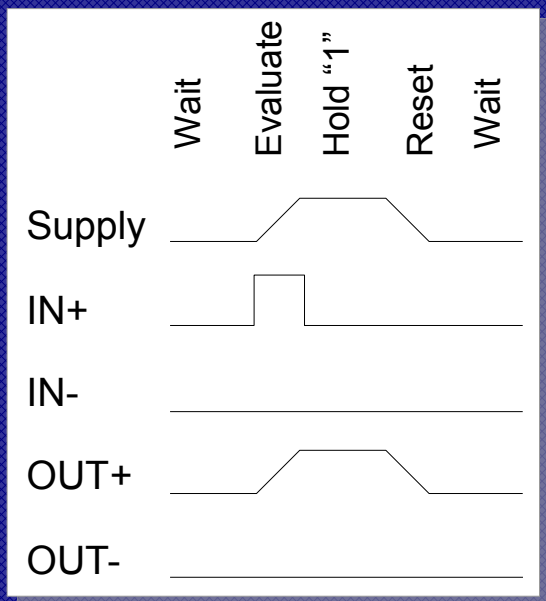

2N-2P Timing Diagram.


Kramer A., Denker J.S. et al, "2nd order adiabatic computation with 2N-2P and 2N-2N2P logic circuits", Proc.1995 Int. Symp. Low power design, pp. 191-196.

# Synchronous Adiabatic Logic

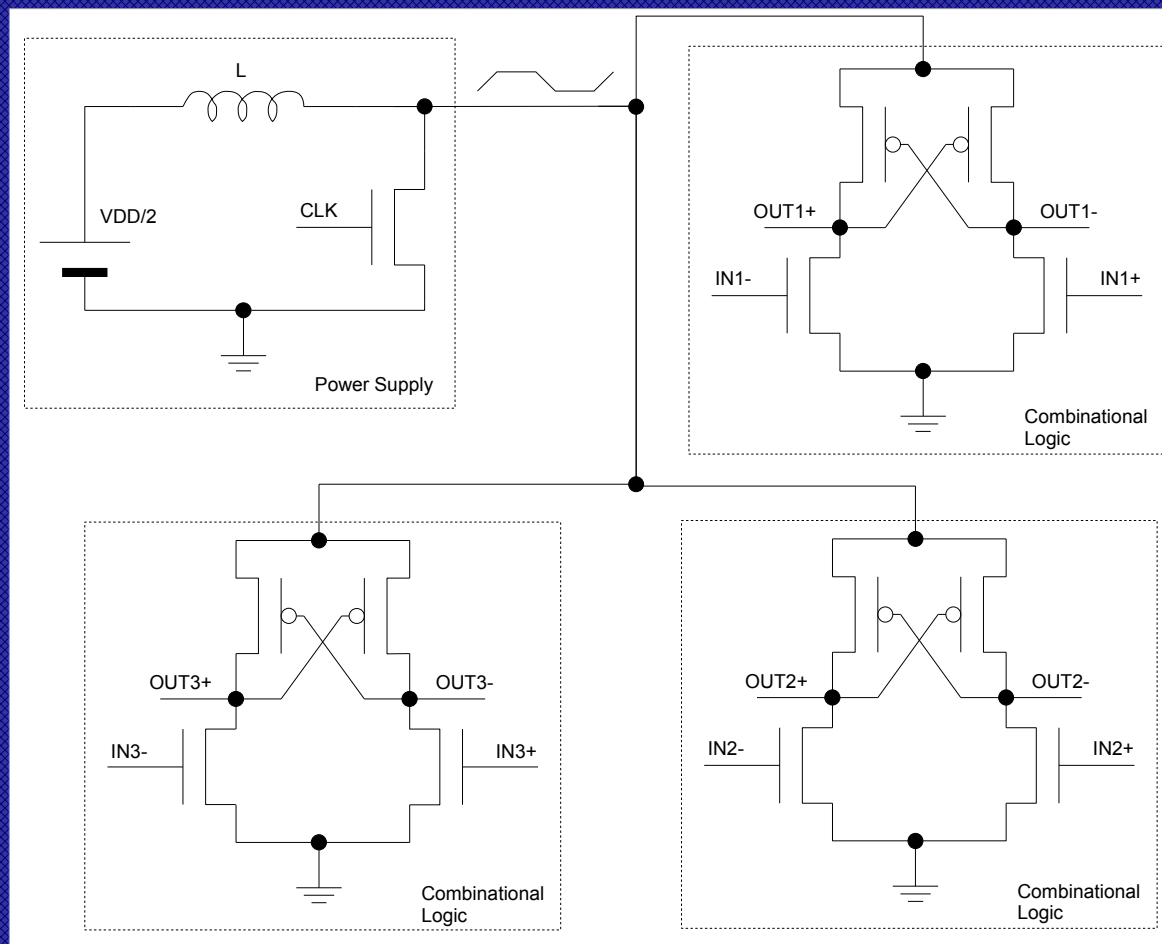

- One fixed frequency - **one global power supply.**
- Might require multiple phases of the power supply.


# Asynchronous Adiabatic Logic

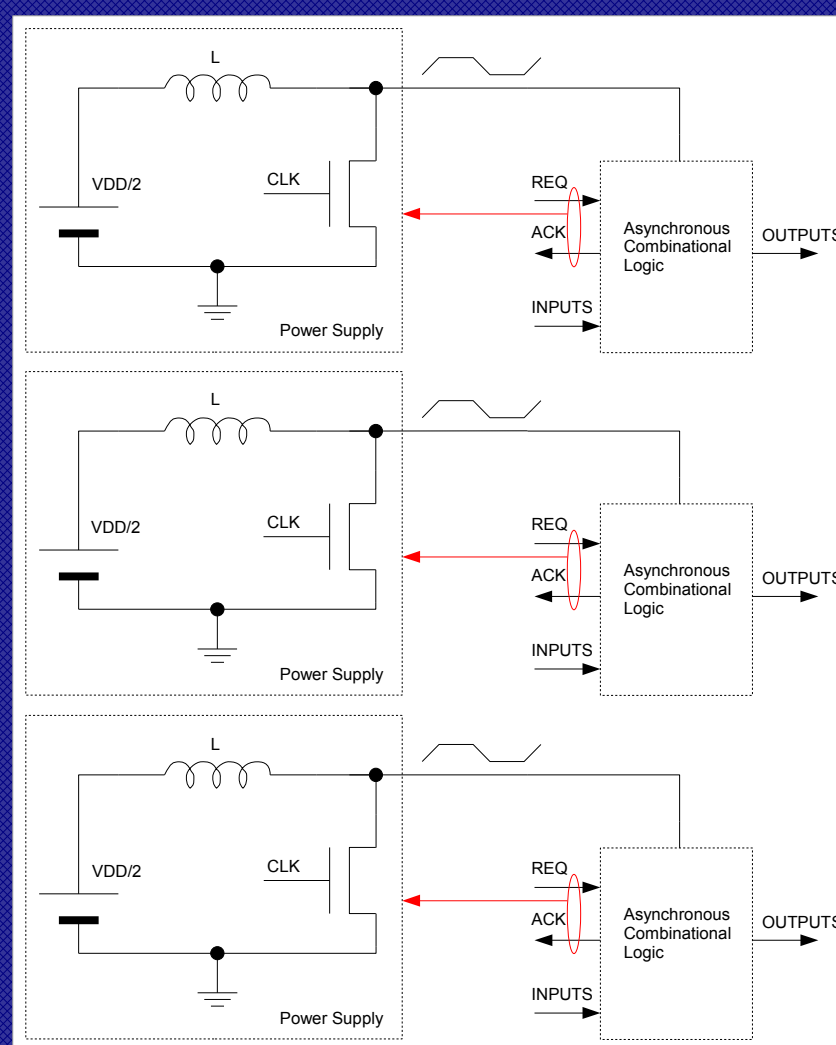

- Multiple frequencies – **many power supplies.**
- Space consuming design approach.




# Asynchronous Adiabatic Logic

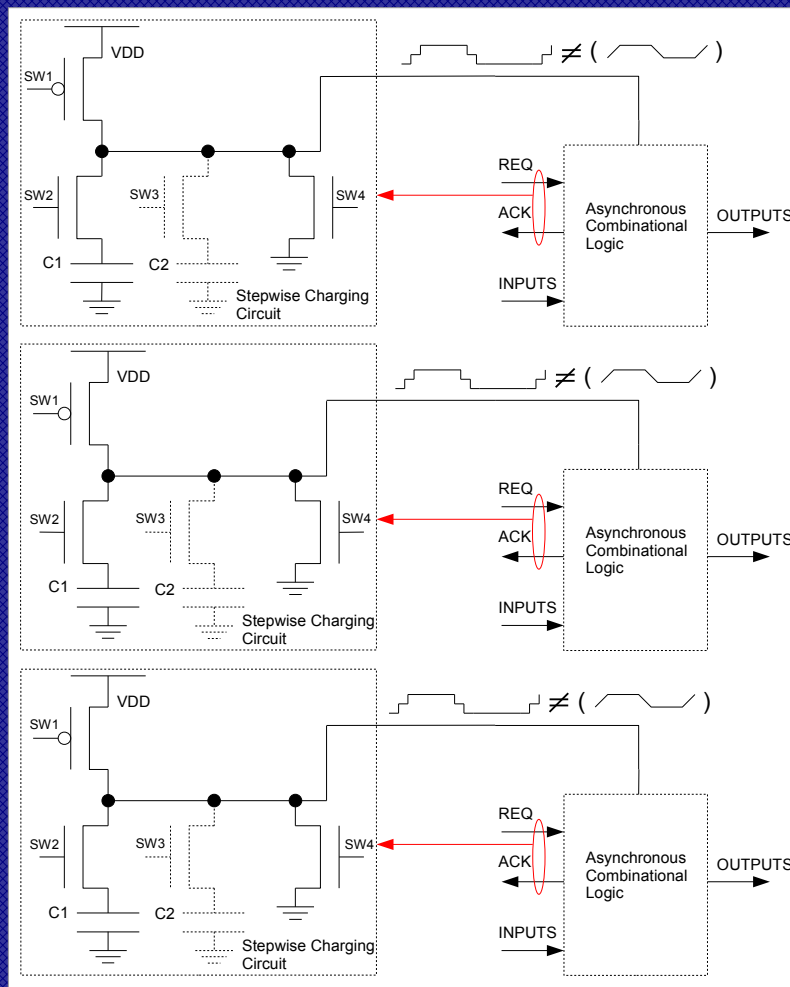

- Using a **stepwise charging circuit**, inductors are eliminated.
- Charging/discharging is **no longer ramp-like**.
- Capacitors still occupy large area on chip.


Willingham D.J. and Kale I., "Asynchronous, quasi-Adiabatic (Asynchrobatic) logic for low-power very wide data width applications", Circuits and Systems, 2004, Proceedings of the 2004 International Symposium on Volume 2, 23-26 May 2004 pp. II - 257-60 Vol.2.

# Proposed Circuit

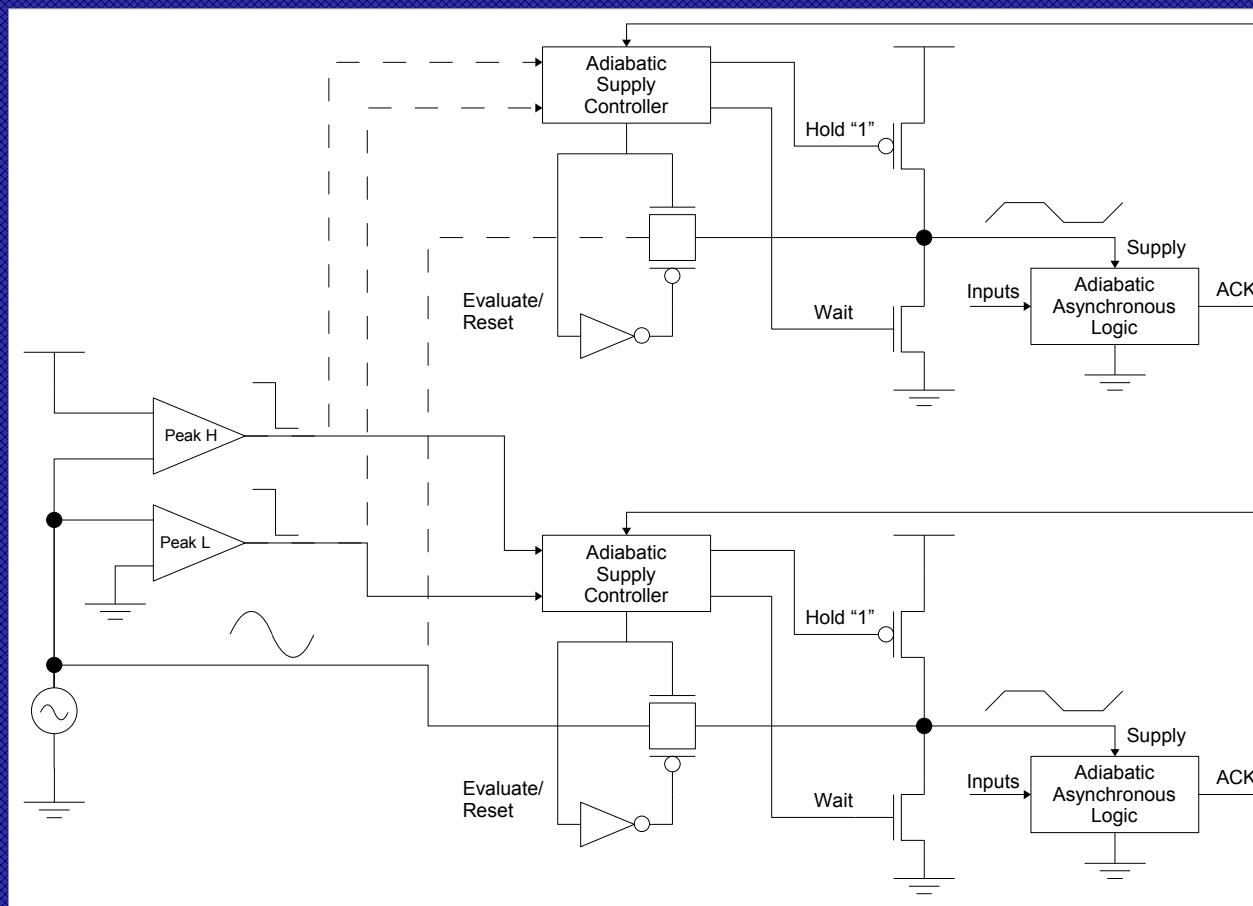


- Only **one inductor-based** supply.
- Ramp-like power supply generated by individual **adiabatic supply controllers**.

# Adiabatic Supply Controller

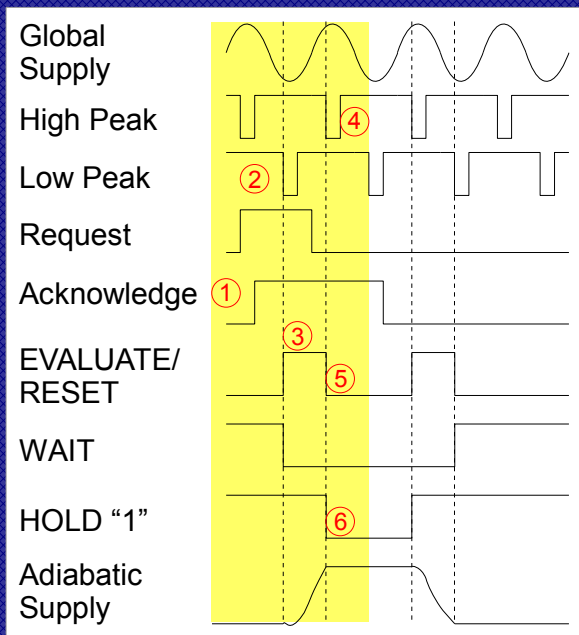


Adiabatic supply controller timing diagram.

Circuit topology.

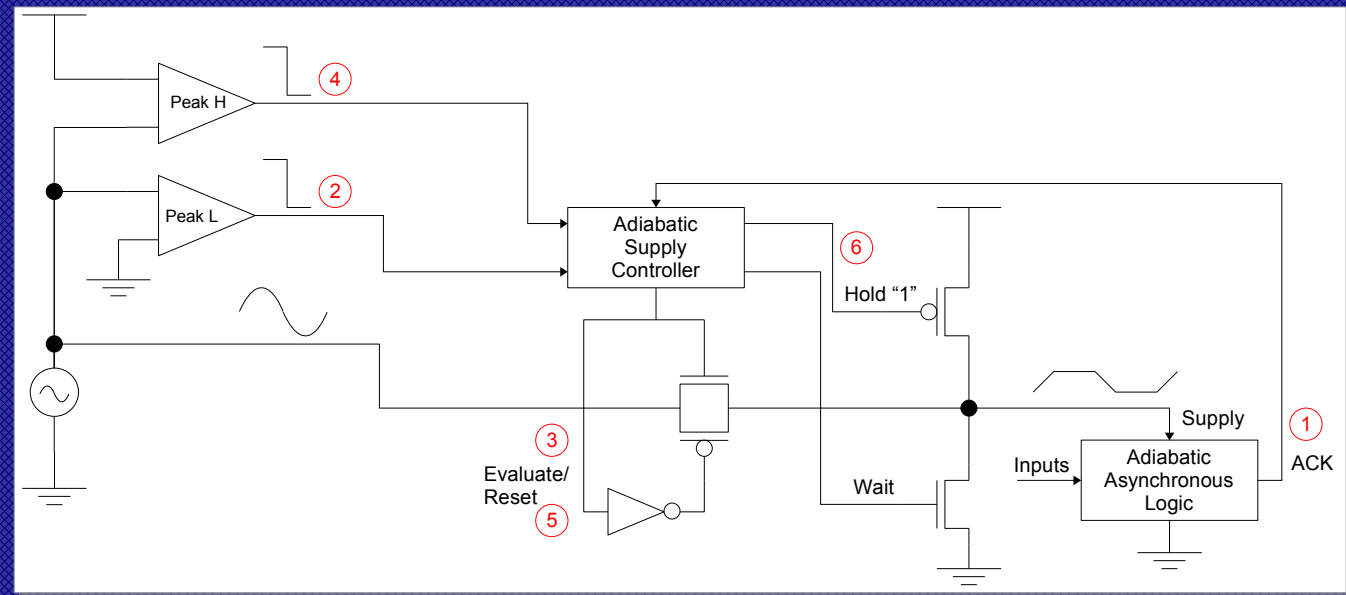


# Adiabatic Supply Controller

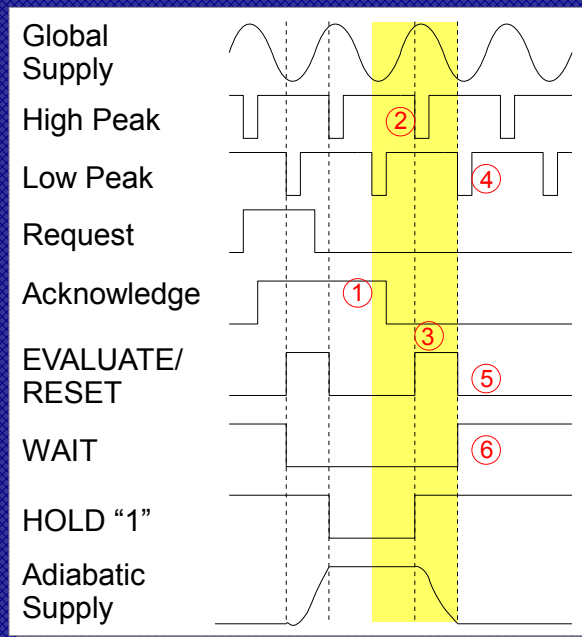


Adiabatic supply controller timing diagram.

Circuit topology.

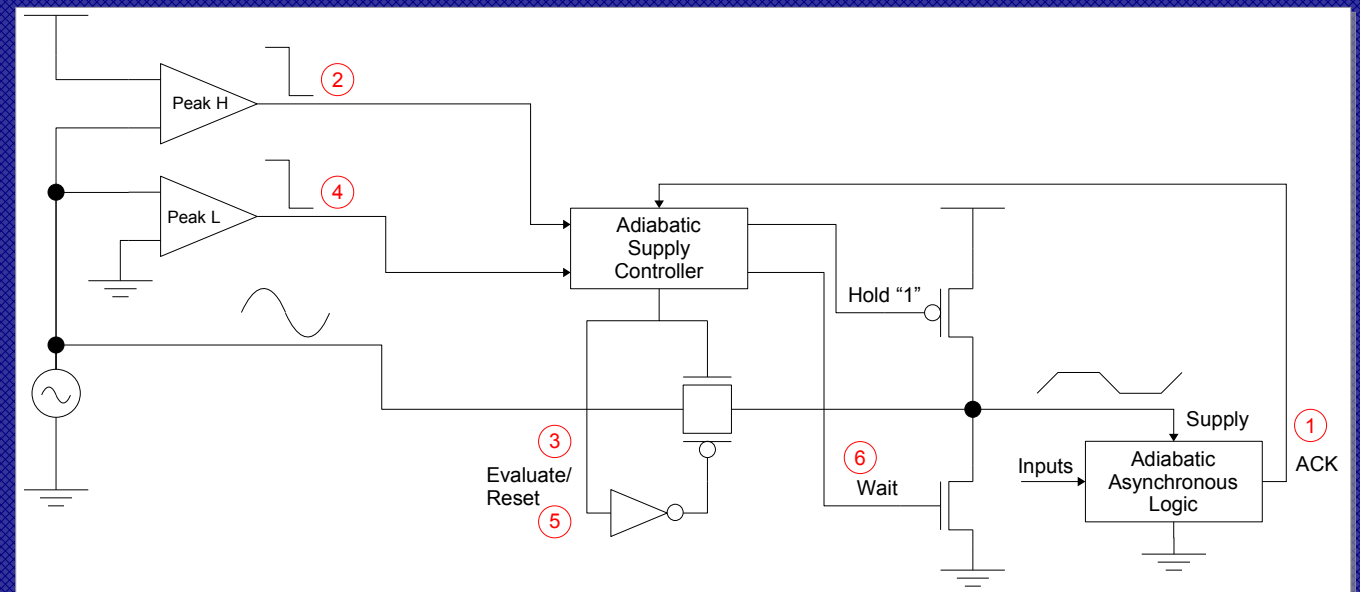


# Adiabatic Supply Controller

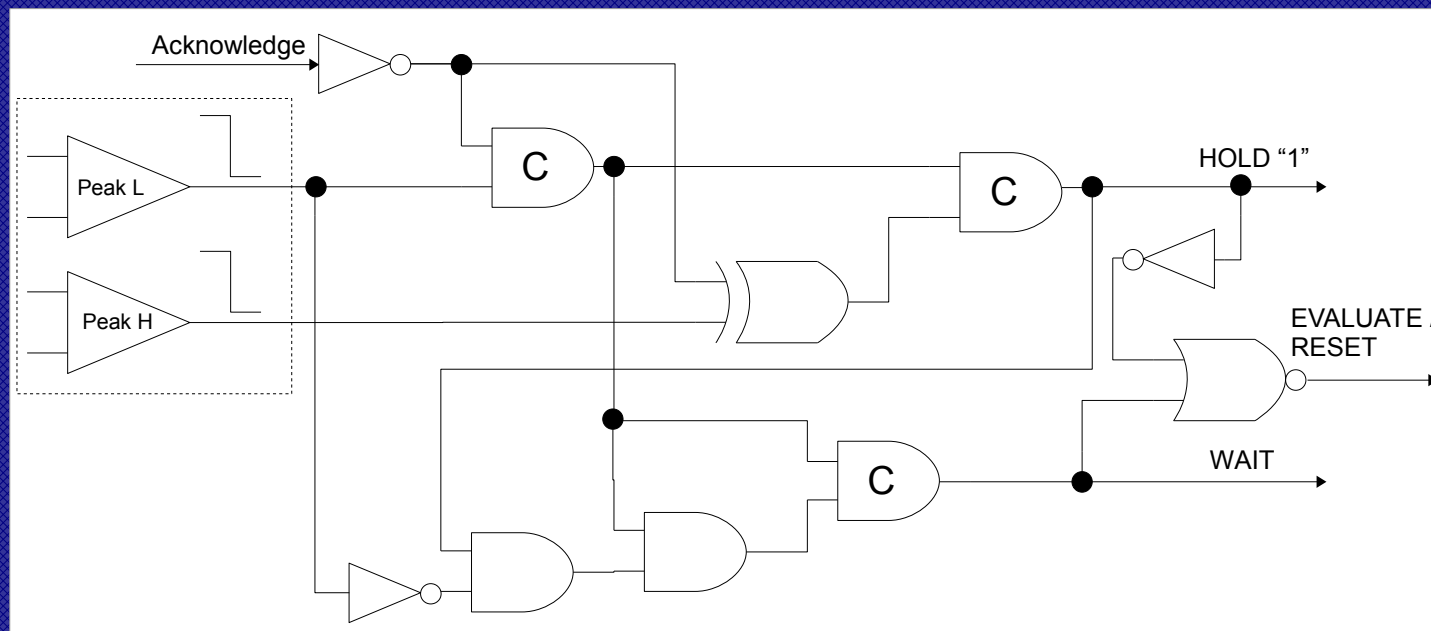

Adiabatic supply controller logic.

# Evaluation

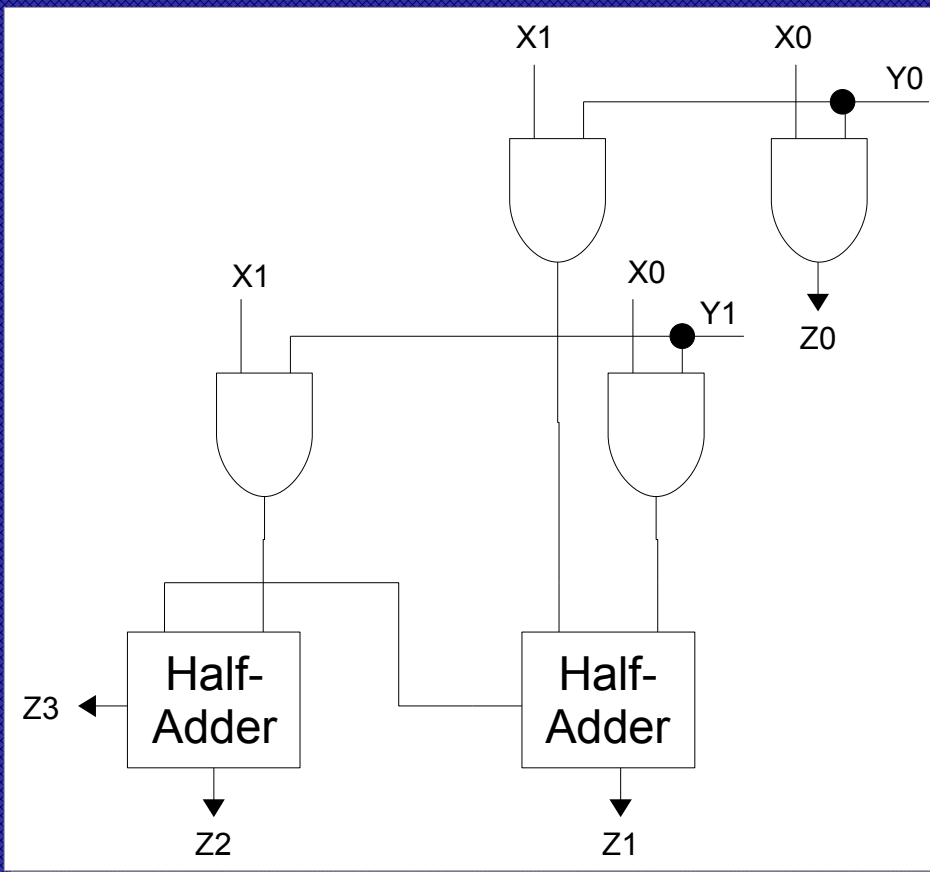


2-bit Multiplier.

- Performance is evaluated by comparing 2,4,5 -bit asynchronous multipliers implemented in both conventional and adiabatic logic.




# Evaluation

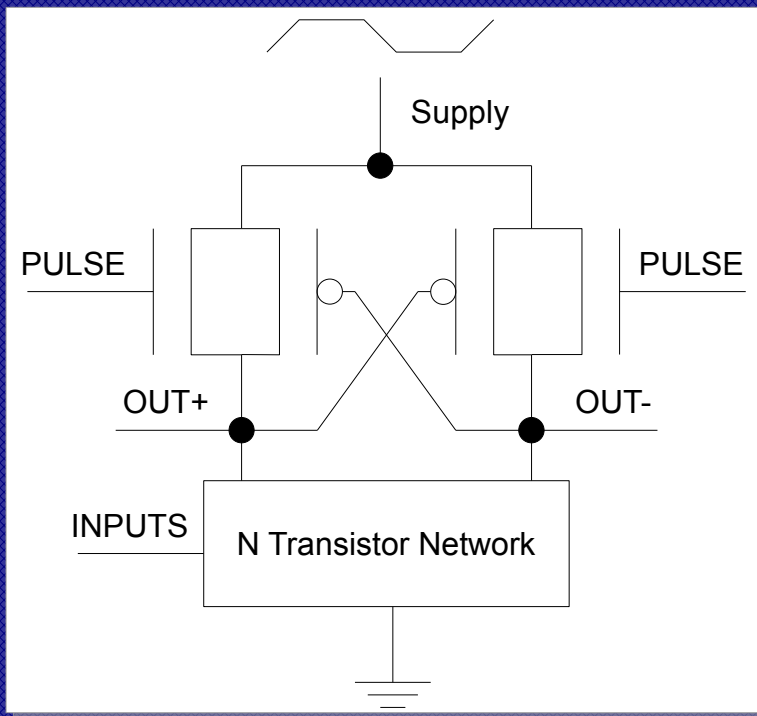

Modified 2N-2P Circuit.

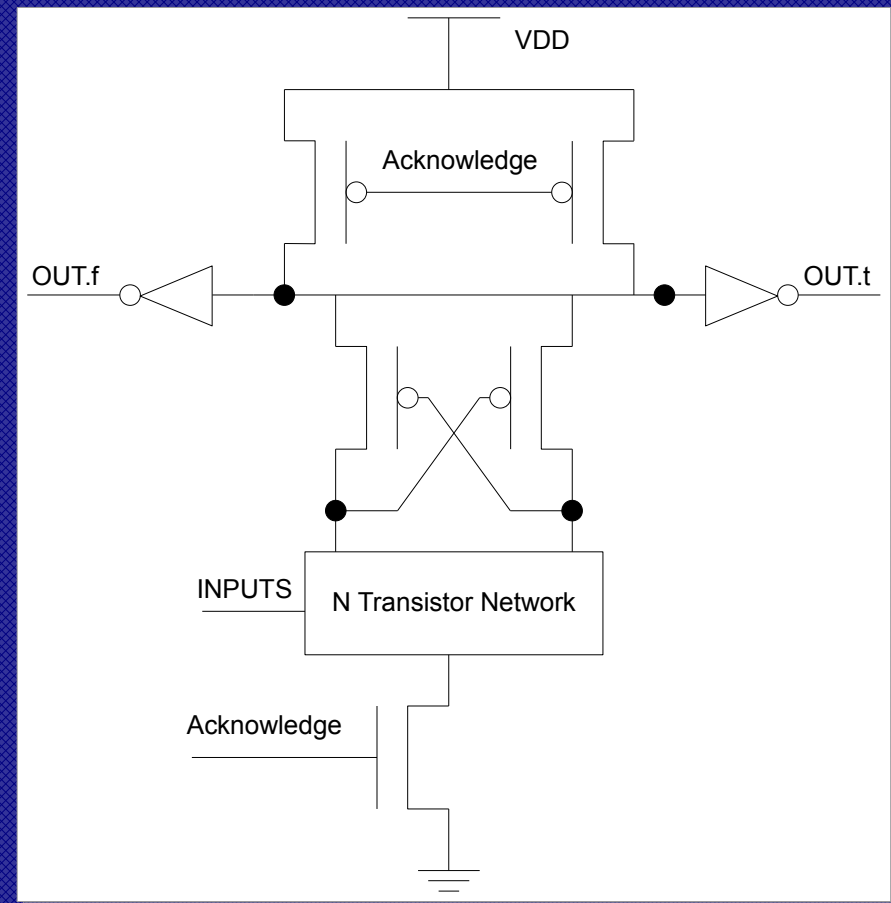Yeh C.C., Lou J.H. and Kuo J.B., "1.5 V CMOS full-swing energy efficient logic (EEL) circuit suitable for low-voltage and low-power VLSI applications", Electronics Letters Volume 33, Issue 16, 31 Jul 1997 pp. 1375 - 1376.




Precharged Differential CMOS Logic.


J Sparso and S Furber, "Principles of asynchronous circuit design - A systems perspective", Kluwer Academic Publishers, 2001.




# Simulation Results

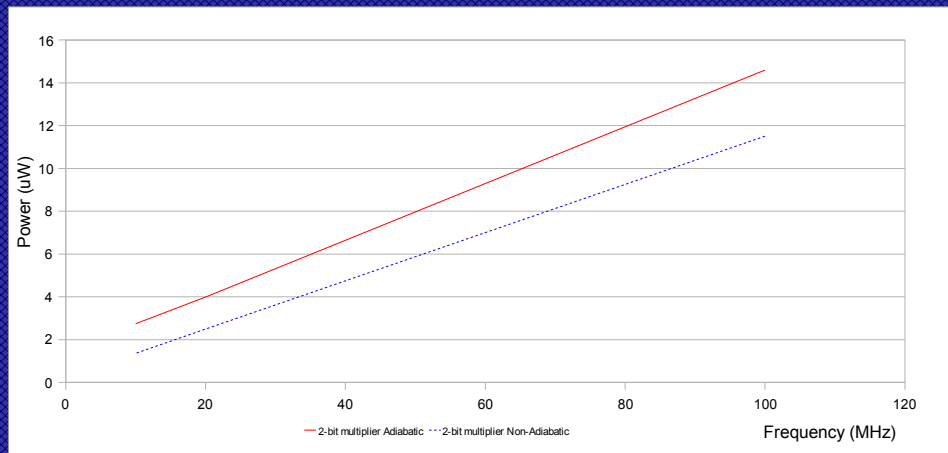

2-bit Multiplier.

 


4-bit Multiplier.

 

5-bit Multiplier.

# Simulation Results

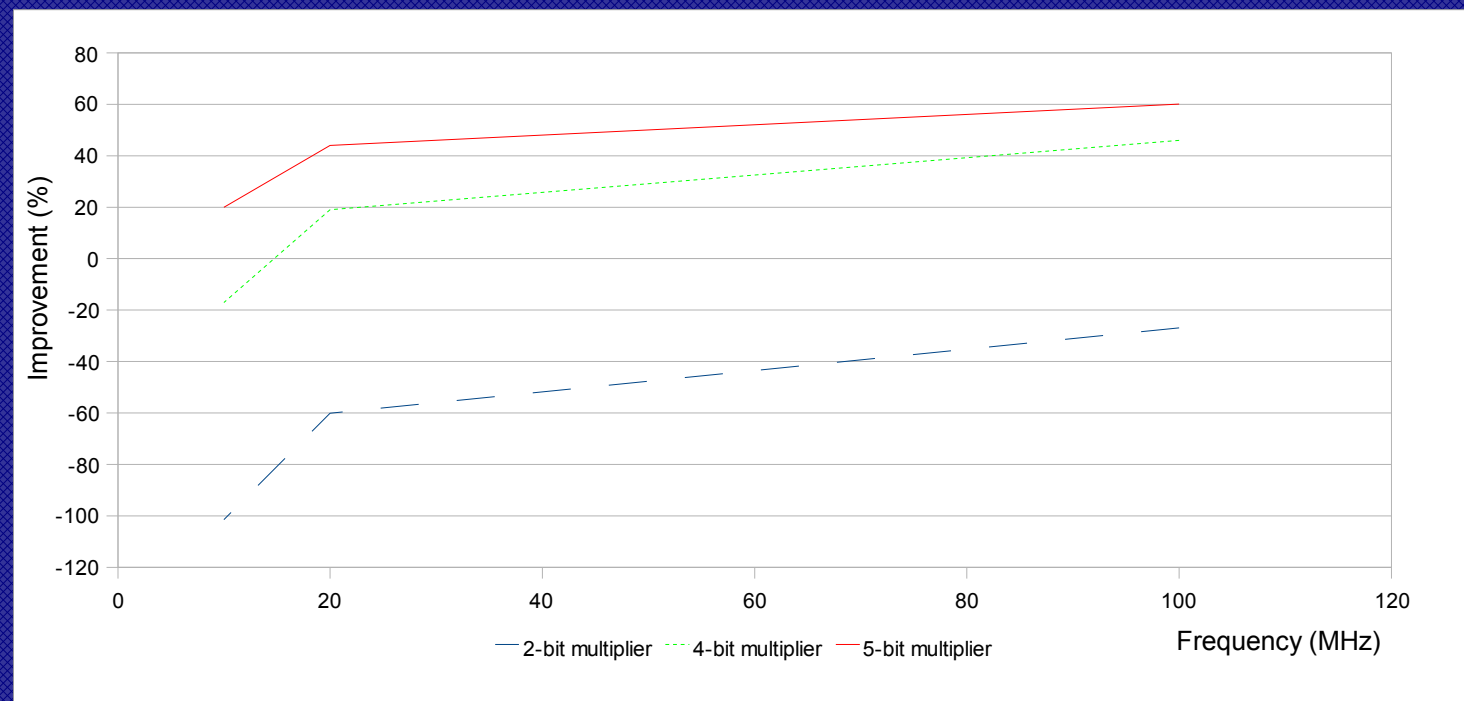


2,4,5-bit Adiabatic Multipliers power improvement over conventional circuit.


# Circuit Weaknesses

- The **operating frequency** of the asynchronous logic blocks **is limited** by the sine-wave supply frequency (can introduce to the handshaking, an additional delay of 3 times the sine-wave period).
- The adiabatic supply controller induces a **power consumption overhead**. This makes the circuit inefficient for simple logic implementations.

# Future

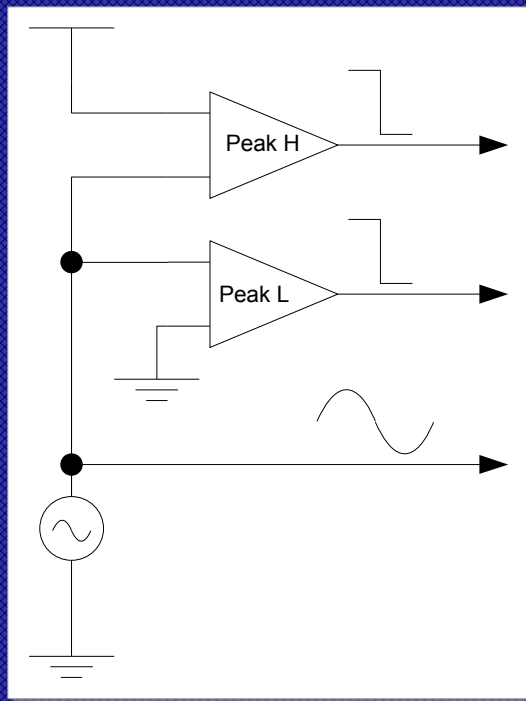

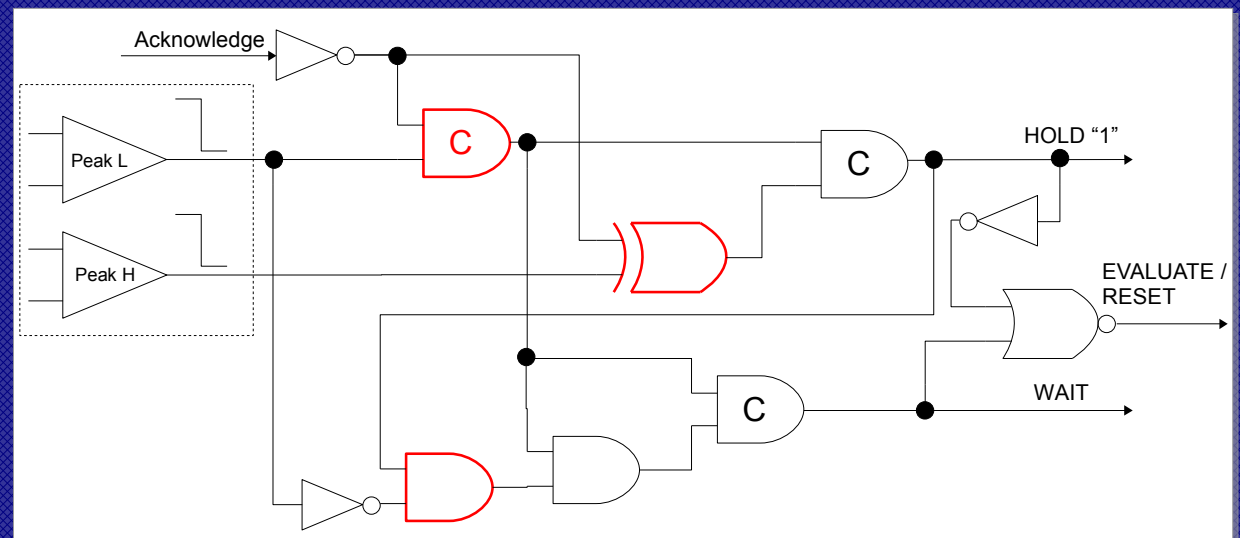Peak detectors/sine-wave generator are ideal.



Metastability.

# Conclusions

- A new approach for the design of asynchronous adiabatic logic was presented.
- Only one inductor-based power supply is required.
- The power improvement over conventional CMOS asynchronous is demonstrated to be more than 60% (can be further improved with more complex computational loads).
- This design approach could benefit applications that require **low-to-medium speed** performance and implement **medium-to-high complexity** logic functions → energy-harvester supplied computational logic.